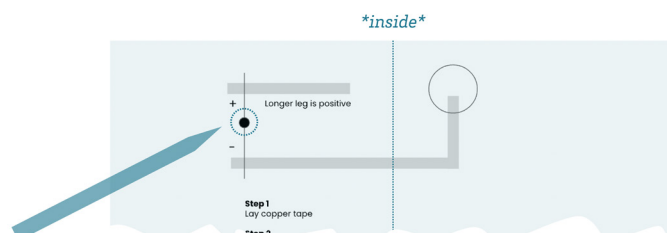


# how to: make an LED card


**1** print and cut the card template – you only need one of the two!



**2** poke the hole for the LED light to fit through




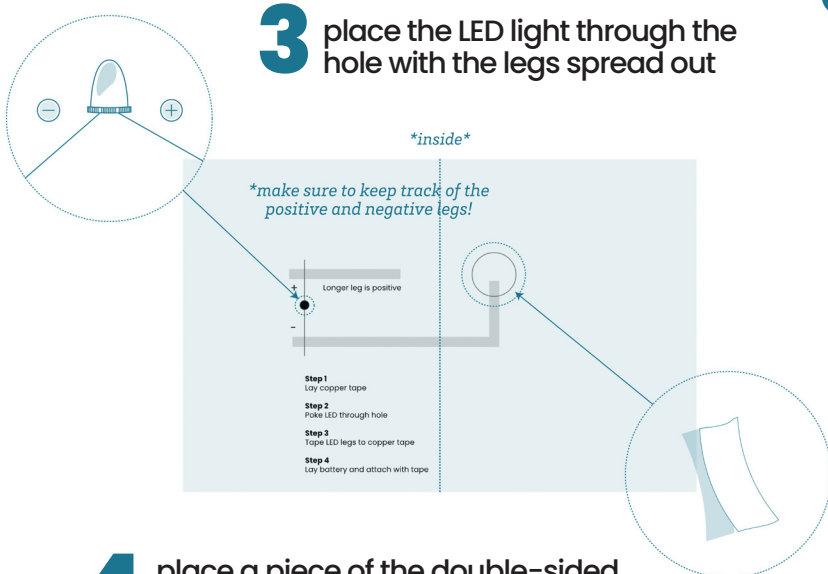**3** place the LED light through the hole with the legs spread out




**5** tape on pieces of copper tape along the gray lines

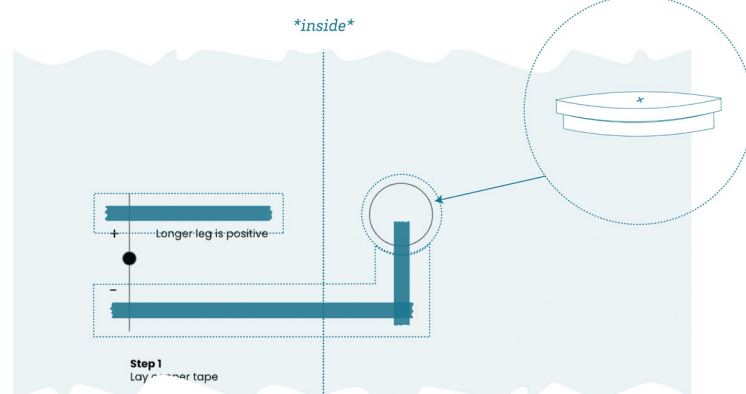**6** tape the battery on top of the circle drawn on the template



**4** place a piece of the double-sided tape where the battery will be placed

**decorate**  
to make it  
even better!

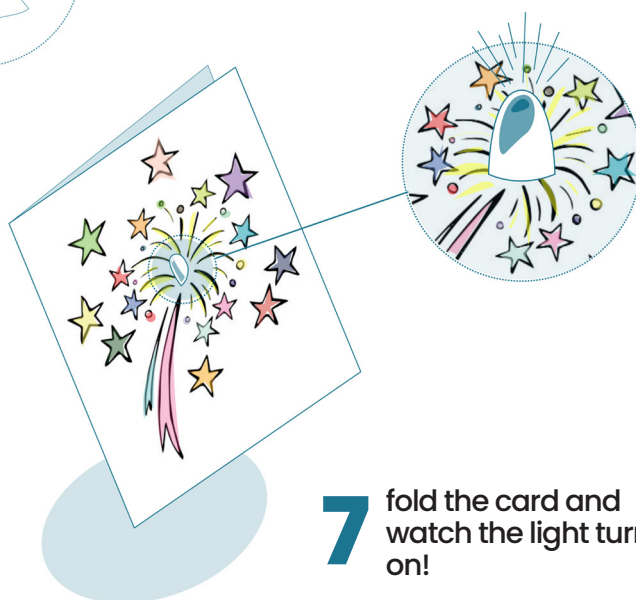

**7** fold the card and watch the light turn on!